

# Grundlagen von VHDL

PHNÖ 3Z5B4SWJ22


Karlheinz Oswald und Bernhard Wess

11. bis 13. März 2024

# Teil I

## Hardware-Beschreibung und -synthese

## Typical FPGA CAD Flow

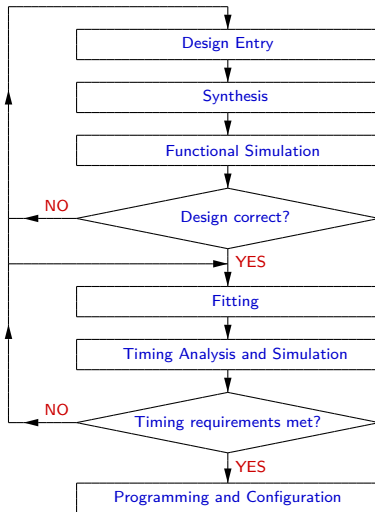

- **Design Entry** - The desired circuit is specified either by using a hardware description language, such as Verilog or VHDL, or by means of a schematic diagram.
- **Synthesis** - The CAD synthesis tool synthesizes the circuit into a netlist that gives the logic elements (LEs) needed to realize the circuit and the connections between the LEs.
- **Functional Simulation** - The synthesized circuit is tested to verify its functional correctness; the simulation does not take into account any timing issues.
- **Fitting** - The CAD fitter tool determines the placement of the LEs defined in the netlist into the LEs in an actual FPGA chip; it also chooses routing wires in the chip to make the required connections between specific LEs.
- **Timing Analysis** - Propagation delays along the various paths in the fitted circuit are analyzed to provide an indication of the expected performance of the circuit.
- **Timing Simulation** - The fitted circuit is tested to verify both its functional correctness and timing.
- **Programming and Configuration** - The designed circuit is implemented in a physical FPGA chip by programming the configuration switches that configure the LEs and establish the required wiring connections.

## Teil II

# Hardware-Beschreibungssprache VHDL

### *The VHDL Acronym*


- VHDL - VHSIC Hardware Description Language
- VHSIC - Very High Speed Integrated Circuit

### *VHDL is a language used for*

- describing the structure and behaviour of digital electronic hardware designs
- testing the functionality of a design


- VHDL is an international standard (1076), regulated by the IEEE.
- The definition of VHDL is non-proprietary.

 VHDL allows separation of the internal and external view of a digital system.



- An **entity** declaration describes the interface of the design to its external environment.
- An **architecture** body describes the functionality of a design.

 
```
-- entity declaration  
entity AOI is  
  
    -- place your entity  
    -- declaration here  
  
end AOI;
```



- The VHDL entity is used to give the design entity its name, in this case AOI.


 
```
-- entity declaration
entity AOI is
    port(A,B,C,D : in  std_logic;
          Z       : out std_logic);
end AOI;
```




- List of ports, each port must also be given a type and an input / output mode.

```
-- entity declaration

entity AOI is
  port(A,B,C,D : in  std_logic;
        Z       : out std_logic);
end AOI;

-- architecture body

 architecture AOI_a of AOI is
begin
  Z <= not((A and B) or (C and D));
end AOI_a;
```




- The architecture is given a name which is different from the entity.
- It must also be associated with an entity declaration.

```
library IEEE;
use IEEE.std_logic_1164.all;

-- entity declaration
entity AOI is
  port(A,B,C,D : in  std_logic;
        Z       : out std_logic);
end AOI;

 -- architecture body
architecture AOI_a of AOI is
begin
  Z <= not((A and B) or (C and D));
end AOI_a;
```



- Type `std_logic` comes from package `std_logic_1164` of the IEEE library.
- A package is a VHDL construct in which new data types, functions, and procedures may be defined.
- `std_logic_1164` is a package for representing digital signals.


```

library IEEE;
use IEEE.std_logic_1164.all;

entity AOI is
  port(A,B,C,D : in  std_logic;
       Z       : out std_logic);
end AOI;

architecture AOI_a of AOI is
  signal I1,I2,I3 : std_logic;
begin
  I1 <= A and B;
  I2 <= C and D;
  I3 <= I1 or I2;
  Z  <= not I3;
end AOI_a;

```

 

- Internal signals are declared before the begin in the architecture.
- Each signal assignment represents a concurrent operation.

### *Library and Package*

```
library ieee;  
use ieee.std_logic_1164.all;
```

- adds additional types, operators, functions, etc. to VHDL

### *Entity Declaration*

```
entity or_gate is  
  port(  
    a,b : in  std_logic;  
    y   : out std_logic  
  );  
end or_gate;
```

- declares the name of the circuit
- specifies the I/O signals

### *Architecture Body*

```
architecture dataflow of or_gate is  
begin  
  y <= a or b;  
end dataflow;
```

- describes operation of the circuit

### *Signal Assignment*

```
signal_name <= expression;
```

### *Example*

```
Z <= A and B;
```

### Signal Assignment

```
signal_name <= expression;
```

### Conditional Signal Assignment

```
signal_name <=  
expression when condition else  
expression when condition else  
expression;
```

### Example

```
Z <= A and B;
```

### Example

```
Z <= A when S="00" else  
      B when S="11" else  
      C;
```

### Signal Assignment

```
signal_name <= expression;
```

### Conditional Signal Assignment

```
signal_name <=  
expression when condition else  
expression when condition else  
expression;
```

### Selected Signal Assignment

```
with selection select  
signal_name <=  
expression when choices,  
expression when choices,  
expression when others;
```

### Example

```
Z <= A and B;
```

### Example

```
Z <= A when S="00" else  
      B when S="11" else  
      C;
```

### Example

```
with S select  
      Z <= A when "00",  
          B when "11",  
          C when others;
```



*Example Statement*



```
r <= a + b + c when m = n else  
    a - b      when m > n else  
    c + 1;
```

*Example Statement*

```

r <= a + b + c when m = n else
    a - b      when m > n else
    c + 1;

```

  *2-to-1 Multiplexer**Block Diagram*


### Example Statement

```


r <= a + b + c when m = n else
    a - b      when m > n else
    c + 1;

```

### 2-to-1 Multiplexer

 

### Block Diagram

 

### Note:

- Infers a priority routing structure.
- A large number of when clauses leads to a long cascading chain.

## Example Statement

```
signal sel: std_logic_vector(1 downto 0);  
.  
.  
with sel select  
  r <= a + b + c when "00",  
    a - b      when "10",  
    c + 1     when others;;
```


## Example Statement

```


signal sel: std_logic_vector(1 downto 0);
.
.
.
with sel select
  r <= a + b + c when "00",
      a - b      when "10",
      c + 1     when others;;

```

## 4-to-1 Multiplexer

 

## Block Diagram

 


## Example Statement

```


signal sel: std_logic_vector(1 downto 0);
.
.
.
with sel select
  r <= a + b + c when "00",
      a - b      when "10",
      c + 1      when others;;

```

## 4-to-1 Multiplexer

 

## Block Diagram

 

## Note:

- Infers a multiplexing structure.
- A large number of choices leads to a wide multiplexer.

### *Format for Architecture Body*

**architecture** *architecture\_name* **of** *entity\_name* **is**

*data type definitions*

*internal signal declarations*

*component declarations*

*function and procedure declarations*

**begin**

*component instantiations*

*processes*

*concurrent statements including*

*signal assignment statements*

*when-else statements*

*with-select-when statements*

**end architecture** *architecture\_name*;

### *Note:*

**architecture** in the end statement is optional.

### Format for Process Statement

**process\_label**: **process**(**sensitivity\_list**)

**variable** **variable\_name**: **type**;

⋮

**variable** **variable\_name**: **type**;

**begin**

*if-then-else statements*

*case-when statements*

*for-loop statements*

*while-loop statements*

*wait statements*

**end process** **process\_label**;

### Note:

- **process\_label** in the end statement is optional.
- An event on any signal of **sensitivity\_list** cause the process to execute.
- Within the process each statement is executed sequentially and only sequential statements can be used in a process.



### *If-Then-Else*

```
if (condition) then
    do stuff
elsif (condition) then
    do more stuff
else
    do other stuff
end if;
```

### *Note:*

- **elsif** and **else** clauses are optional.
- Incompletely specified **if** statement (no **else**) implies a memory element.

### If-Then-Else

```
if (condition) then
    do stuff
elsif (condition) then
    do more stuff
else
    do other stuff
end if;
```

### Example

```
if (S="00") then
    Z <= A;
elsif (S="11") then
    Z <= B;
else
    Z <= C;
end if;
```

### Note:

- **elsif** and **else** clauses are optional.
- Incompletely specified **if** statement (no **else**) implies a memory element.

### Case-When

```
case expression is
  when value =>
    do stuff
  when value =>
    do more stuff
  when others =>
    do other stuff
end case;
```

### Case-When

```
case expression is
  when value =>
    do stuff
  when value =>
    do more stuff
  when others =>
    do other stuff
end case;
```

### Example

```
case S is
  when "00" =>
    Z <= A;
  when "11" =>
    Z <= B;
  when others =>
    Z <= C;
end case;
```

## Function Table

r	pcode
1---	100
01--	011
001-	010
0001	001
0000	000

## Conditional Signal Assignment

```
architecture csa_behavior of prio_enc is
begin
  pcode <= "100" when (r(4)='1') else
           "011" when (r(3)='1') else
           "010" when (r(2)='1') else
           "001" when (r(1)='1') else
           "000";
end csa_behavior;
```

## Entity Declaration

```
entity prio_enc is
  port( r      : in  std_logic_vector(4 downto 1);
        pcode : out std_logic_vector(2 downto 0)
      );
end prio_enc;
```

## Selected Signal Assignment

```
architecture ssa_behavior of prio_enc is
begin
  with r select
    pcode <= "100" when "1000"|"1001"|"1010"|"1011"|
                    "1100"|"1101"|"1110"|"1111"|,
           "011" when "0100"|"0101"|"0110"|"0111"|,
           "010" when "0010"|"0011"|,
           "001" when "0001"|,
           "000" when others;
end ssa_behavior;
```

## Function Table

r	pcode
1---	100
01--	011
001-	010
0001	001
0000	000

## If Statement

```
architecture if_behavior of prio_enc is
begin
  process(r)
  begin
    if (r(4)='1') then
      pcode <= "100";
    elsif (r(3)='1') then
      pcode <= "011";
    elsif (r(2)='1') then
      pcode <= "010";
    elsif (r(1)='1') then
      pcode <= "001";
    else
      pcode <= "000";
    end if;
  end process;
end if_behavior;
```

## Entity Declaration

```
entity prio_enc is
  port( r      : in  std_logic_vector(4 downto 1);
        pcode : out std_logic_vector(2 downto 0)
      );
end prio_enc;
```

## Case Statement

```
architecture case_behavior of prio_enc is
begin
  process(r)
  begin
    case r is
      when "1000"|"1001"|"1010"|"1011"|
           "1100"|"1101"|"1110"|"1111" =>
        pcode <= "100";
      when "0100"|"0101"|"0110"|"0111" =>
        pcode <= "011";
      when "0010"|"0011" =>
        pcode <= "010";
      when "0001" =>
        pcode <= "001";
      when others =>
        pcode <= "000";
    end case;
  end process;
end case_behavior;
```

### Unintended Memory

```
process(a)
begin
  if (a > b) then
    gt <= '1';
  elsif (a = b) then
    eq <= '1';
  end if;
end process;
```

### Correct Code

```
process(a,b)
begin
  if (a > b) then
    gt <= '1';
    eq <= '0';
  elsif (a = b) then
    gt <= '0';
    eq <= '1';
  else
    gt <= '0';
    eq <= '0';
  end if;
end process;
```

### Correct Code

```
process(a,b)
begin
  gt <= '0';
  eq <= '0';
  if (a > b) then
    gt <= '1';
  elsif (a = b) then
    eq <= '1';
  end if;
end process;
```

### Rules to prevent unintended memory

- Include all input signals in the sensitivity list.
- Include the else branch in an if statement.
- Assign a value to every signal in every branch.

## Predefined Data Types

- integer: minimal range is from  $-(2^{31} - 1)$  to  $2^{31} - 1$ 
  - subtypes: natural and positive
- boolean: defined as (false, true)
- bit: defined as ('0', '1')
- bit\_vector: defined als a one-dimensional array with elements of bit data type.

## IEEE std\_logic\_1164 Package

- The std\_logic data type consists of nine possible values:  
( 'U', 'X', '0', '1', 'Z', 'W', 'L', 'H', '-' )
- The std\_logic\_vector data type is an array of elements with the std\_logic data type.
- Include the necessary library and use statements before the entity declaration:

```
library ieee;  
use ieee.std_logic_1164.all;
```



## IEEE numeric\_std Package

- New data types: signed and unsigned
  - Better control over the underlying hardware than with the integer data type.

- Required library statements:

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

- Overloaded operators

- abs, \*, /, mod, rem, +, -
- Operators with two operands:  
unsigned and unsigned, unsigned and natural, signed and signed,  
signed and integer

- Several new functions

- shift\_left, shift\_right, rotate\_left, rotate\_right
- Type conversion: to\_unsigned, to\_signed, to\_integer

Operator	Description	Data type of a	Data type of b	Data type of result
a ** b	exponentiation	int	int	int
abs a	absolute value	int		int
a * b	multiplication	int	int	int
a / b	division	int	int	int
a mod b	modulo	int	int	int
a rem b	remainder	int	int	int
+ a	identity	int		int
- a	negation	int		int
a + b	addition	int	int	int
a - b	subtraction	int	int	int
a & b	concatenation	array, element	array, element	array
a sll b	shift left log.	bitv	int	bitv
a srl b	shift right log.	bitv	int	bitv
a sla b	shift left arith.	bitv	int	bitv
a sra b	shift right arith.	bitv	int	bitv
a rol b	rotate left	bitv	int	bitv
a ror b	rotate right	bitv	int	bitv

Operator	Description	Data type of a	Data type of b	Data type of result
a = b	equal to	any	same as a	boo
a /= b	not equal to	any	same as a	boo
a < b	less than	scalar, array	same as a	boo
a <= b	l. th. or eq. to	scalar, array	same as a	boo
a > b	greater than	scalar, array	same as a	boo
a >= b	g. th. or eq. to	scalar, array	same as a	boo
not a	negation	boo, bit, bitv		same as a
a and b	and	boo, bit, bitv	same as a	same as a
a or b	and	boo, bit, bitv	same as a	same as a
a xor b	and	boo, bit, bitv	same as a	same as a
a nand b	and	boo, bit, bitv	same as a	same as a
a nor b	and	boo, bit, bitv	same as a	same as a
a xnor b	and	boo, bit, bitv	same as a	same as a

## Relational Operators

- The comparison procedure starts from the leftmost element and continues until a result can be established.
- For example, the following operations return true:  
"011"="011", "011">"010"

## Concatenation Operator


- We can combine elements and smaller arrays to form a larger array.
- Example: "00" & a(7 downto 2)

## Array Aggregate

- Assignment: a <= "10100000"
- Positional Association: a <= ('1', '0', '1', '0', '0', '0', '0', '0')
- Named Association:
  - a <= (7=>'1', 6=>'0', 5=>'1', 4=>'0', 3=>'0', 2=>'0', 1=>'0', 0=>'0')
  - a <= (7|5=>'1', 6|4|3|2|1|0=>'0')
  - a <= (7|5=>'1', others=>'0')

# Teil III

## Hierarchisches VHDL-Design

 *Truth Table*

A	B	Ci	S	Co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## Sum


		B Ci			
		00	01	11	10
A	0	0	1	0	1
	1	1	0	1	0

## Carry Out

		B Ci			
		00	01	11	10
A	0	0	0	1	1
	1	0	1	1	1

$$\begin{aligned}
 S &= A \cdot \bar{B} \cdot \bar{C}_i + \bar{A} \cdot \bar{B} \cdot C_i + A \cdot B \cdot C_i + \bar{A} \cdot B \cdot \bar{C}_i \\
 &= (A \cdot \bar{B} + \bar{A} \cdot B) \cdot \bar{C}_i + (A \cdot B + \bar{A} \cdot \bar{B}) \cdot C_i \\
 &= (A \oplus B) \cdot \bar{C}_i + (\overline{A \oplus B}) \cdot C_i \\
 &= A \oplus B \oplus C_i
 \end{aligned}$$
 
$$C_o = A \cdot B + A \cdot C_i + B \cdot C_i$$




### VHDL Code


```
library IEEE;
use IEEE.std_logic_1164.all;

entity FA is
    port(A,B,Ci : in  std_logic;
         S,Co   : out std_logic);
end FA;

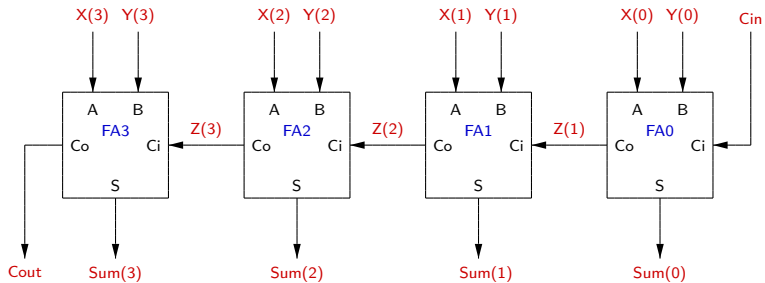architecture FA_a of FA is
begin
    S <= A xor B xor Ci;
    Co <= (A and B) or (A and Ci) or (B and Ci);
end FA_a;
```



*Schematic*

 

## VHDL Code

```

library IEEE;
use IEEE.std_logic_1164.all;

entity Adder4 is
  port(X, Y : in std_logic_vector(3 downto 0);
       Cin : in std_logic;
       Sum : out std_logic_vector(3 downto 0);
       Cout : out std_logic);
end Adder4;


architecture Adder4_a of Adder4 is

  component FA
    port(A,B,Ci : in std_logic;
         S,Co : out std_logic);
  end component;

  signal Z : std_logic_vector(3 downto 1);

begin
  FA0: FA port map (X(0), Y(0), Cin, Sum(0), Z(1));
  FA1: FA port map (X(1), Y(1), Z(1), Sum(1), Z(2));
  FA2: FA port map (X(2), Y(2), Z(2), Sum(2), Z(3));
  FA3: FA port map (X(3), Y(3), Z(3), Sum(3), Cout);
end Adder4_a;

```

 


## Test Bench

```

library IEEE;
use IEEE.std_logic_1164.all;

entity tb_adder4 is
end tb_adder4;

architecture tb_adder4_a of tb_adder4 is
  component Adder4
    port(X, Y : in std_logic_vector(3 downto 0);
         Cin : in std_logic;
         Sum : out std_logic_vector(3 downto 0);
         Cout : out std_logic);
  end component;
  signal X, Y : std_logic_vector(3 downto 0);
  signal Cin : std_logic;
  signal Sum : std_logic_vector(3 downto 0);
  signal Cout : std_logic;
begin
  UUT: Adder4 port map (X,Y,Cin,Sum,Cout);
  stimulus: process
  begin
    Cin <= '0';
    X <= "1011";
    Y <= "0100";
    wait for 100 ns;
    Cin <= '1';
    wait for 100 ns;
  end process;
end tb_adder4_a;
  
```

 

## VHDL Code

```

library IEEE;
use IEEE.std_logic_1164.all;

entity RCAdder is
  generic(n : integer);
  port(X, Y : in std_logic_vector(n-1 downto 0);
        Cin : in std_logic;
        Sum : out std_logic_vector(n-1 downto 0);
        Cout : out std_logic);
end RCAdder;

architecture RCAdder_a of RCAdder is

  component FA
    port(a,b,ci : in std_logic;
         s,co : out std_logic);
  end component;

  signal Z : std_logic_vector(n downto 0);

begin
  Z(0) <= Cin;
  Cout <= Z(n);
  AddGen: for i in 0 to n-1 generate
    FAn: FA port map (X(i), Y(i), Z(i), Sum(i), Z(i+1));
  end generate;
end RCAdder_a;

```

## Test Bench

```
library IEEE;
use IEEE.std_logic_1164.all;

entity tb_RCadder is
end tb_RCadder;

architecture tb_RCadder_a of tb_RCadder is

component RCadder
  generic(n : integer);
  port(X, Y : in std_logic_vector(n downto 0);
        Cin : in std_logic;
        Sum : out std_logic_vector(n downto 0);
        Cout : out std_logic
        );
end component;

constant n : integer := 5;


signal X, Y : std_logic_vector(n-1 downto 0);
signal Cin : std_logic;
signal Sum : std_logic_vector(n-1 downto 0);
signal Cout : std_logic;

begin


UUT: RCadder generic map (n) port map (X,Y,Cin,Sum,Cout);
```

```
stimulus: process
begin
  Cin <= '0';
  X <= "01010";
  Y <= "00100";
  wait for 100 ns;
  Cin <= '1';
  wait for 100 ns;
end process;

end tb_RCadder_a;
```

 


## Schematic

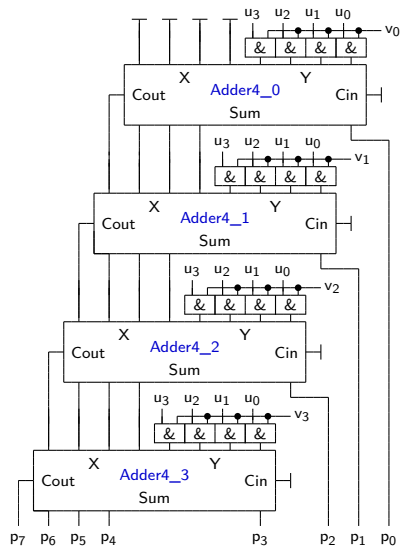

## Example

$$\begin{array}{r}
 1011 \times 1101 \\
 \hline
 1011 \\
 0000 \\
 1011 \\
 1011 \\
 \hline
 10001111
 \end{array}$$

## Schematic

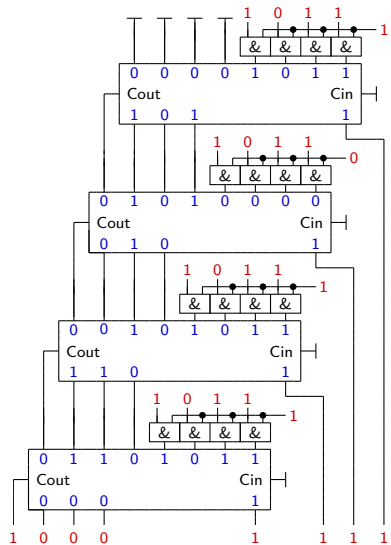

*VHDL Code*





## VHDL Code

```

library IEEE;
use IEEE.std_logic_1164.all;

entity mult4 is
  port(U, V : in std_logic_vector(3 downto 0);
        P   : out std_logic_vector(7 downto 0)
        );
end mult4;

architecture mult4_a of mult4 is

  component and4
    port(A : in std_logic_vector(3 downto 0);
          x : in std_logic;
          Z : out std_logic_vector(3 downto 0)
          );
  end component;

  component Adder4
    port(X, Y : in std_logic_vector(3 downto 0);
          Cin : in std_logic;
          Sum : out std_logic_vector(3 downto 0);
          Cout : out std_logic
          );
  end component;


```

```

  signal X0, X1,
          X2, X3 : std_logic_vector(3 downto 0);
  signal Y0, Y1,
          Y2, Y3 : std_logic_vector(3 downto 0);
  signal S0, S1,
          S2, S3 : std_logic_vector(3 downto 0);
  signal C0, C1,
          C2, C3 : std_logic;

begin
  And_0: and4 port map (U, V(0), Y0);
  And_1: and4 port map (U, V(1), Y1);
  And_2: and4 port map (U, V(2), Y2);
  And_3: and4 port map (U, V(3), Y3);
  Add_0: Adder4 port map (X0, Y0, '0', S0, C0);
  Add_1: Adder4 port map (X1, Y1, '0', S1, C1);
  Add_2: Adder4 port map (X2, Y2, '0', S2, C2);
  Add_3: Adder4 port map (X3, Y3, '0', S3, C3);
  X0 <= "0000";
  X1 <= C0&S0(3 downto 1);
  X2 <= C1&S1(3 downto 1);
  X3 <= C2&S2(3 downto 1);
  P <= C3&S3&S2(0)&S1(0)&S0(0);
end mult4_a;

```

 

## Test Bench

```

library IEEE;
use IEEE.std_logic_1164.all;

entity tb_mult4 is
end tb_mult4;

architecture tb_mult4_a of tb_mult4 is
  component mult4
    port(U, V : in std_logic_vector(3 downto 0);
         P   : out std_logic_vector(7 downto 0));
  end component;
  signal U, V : std_logic_vector(3 downto 0);
  signal P   : std_logic_vector(7 downto 0);
begin
  UUT: mult4 port map (U,V,P);
  stimulus: process
  begin
    U <= "1011";
    V <= "0100";
    wait for 100 ns;
    U <= "1001";
    V <= "0101";
    wait for 100 ns;
  end process;
end tb_mult4_a;
  
```


# Teil IV

## VHDL Design Example


## Problem


Construct a circuit that generates a leap year flag. Use binary coded decimal (BCD) notation for the year, four decimal digits of 4 bits each.

## Leap Year Calculation

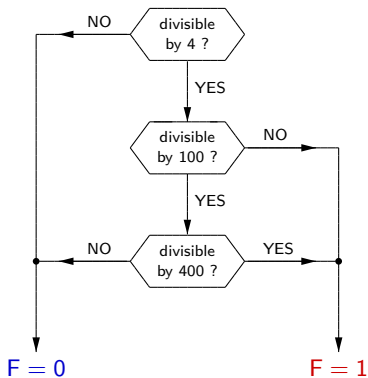

## VHDL Code

 

 

## VHDL Code

```


library IEEE;
use IEEE.std_logic_1164.all;


entity div4_check is
  port(hi,lo : in  std_logic_vector(3 downto 0);
       res  : out std_logic);
end div4_check;

architecture div4_check_a of div4_check is
  signal n,v,a,z,s : std_logic;
  signal sel       : std_logic_vector(4 downto 0);
begin
  sel <= hi(0)&lo;
  with sel select
    n <= '1' when "00000",
      '0' when others;
  with sel select
    v <= '1' when "00100",
      '0' when others;
  with sel select
    a <= '1' when "01000",
      '0' when others;
  with sel select
    z <= '1' when "10010",
      '0' when others;
  with sel select
    s <= '1' when "10110",
      '0' when others;
  res <= n or v or a or z or s;
end div4_check_a;

```

## VHDL Code

 

 

## VHDL Code

```

library IEEE;
use IEEE.std_logic_1164.all;

entity LeapYearFlag is
    port(T,H,Z,E : in std_logic_vector(3 downto 0);
         F       : out std_logic);
end LeapYearFlag;

architecture LeapYearFlag_a of LeapYearFlag is

    component div4_check
        port(nm,nl : in  std_logic_vector(3 downto 0);
             res   : out std_logic);
    end component;


    signal div_by_4lo, div_by_100,
           div_by_4hi : std_logic;
    signal sel
           : std_logic_vector(7 downto 0);

begin
    Test4lo: div4_check port map (Z,E,div_by_4lo);
    sel <= Z&E;
    with sel select
        div_by_100 <= '1' when "00000000",
                    '0' when others;
    Test4hi: div4_check port map (T,H,div_by_4hi);
    F <= (div_by_4lo and
          (not div_by_100)) or (div_by_4hi and div_by_100);
end LeapYearFlag_a;

```



## Test Bench

 

```

library IEEE;
use IEEE.std_logic_1164.all;

entity tb_LeapYearFlag is
end tb_LeapYearFlag;


architecture tb_LeapYearFlag_a of tb_LeapYearFlag is
  component LeapYearFlag is
    port(T, H, Z, E : in std_logic_vector(3 downto 0);
         F          : out std_logic);
  end component;
  signal T, H, Z, E : std_logic_vector(3 downto 0);
  signal F          : std_logic;
begin
  UUT: LeapYearFlag port map (T,H,Z,E,F);
  stimulus: process
  begin
    T <= "0010"; H <= "0000"; Z <= "0000"; E <= "1000";
    wait for 100 ns;
    T <= "0010"; H <= "0000"; Z <= "0000"; E <= "0011";
    wait for 100 ns;
    T <= "0010"; H <= "0000"; Z <= "0000"; E <= "0000";
    wait for 100 ns;
    T <= "0010"; H <= "0001"; Z <= "0000"; E <= "0000";
    wait for 100 ns;
  end process;
end tb_LeapYearFlag_a;


```

# Teil V


## Finite State Machines

## Block Diagram

 


 *Node*


## ASM Block

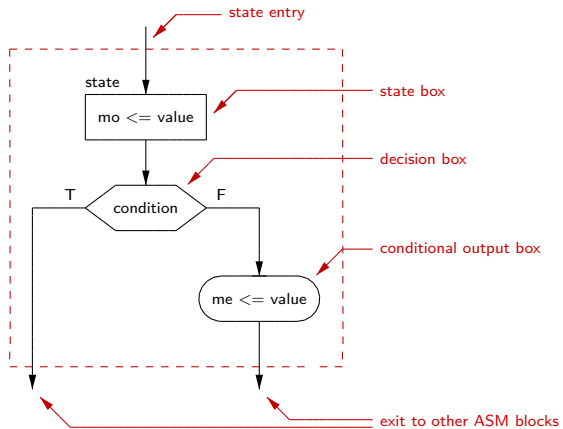


## State Diagram

 


## ASM Chart

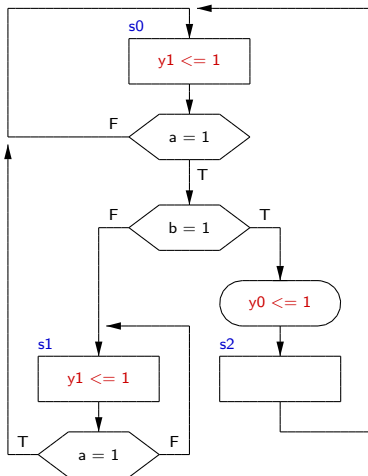


## Timing Diagram

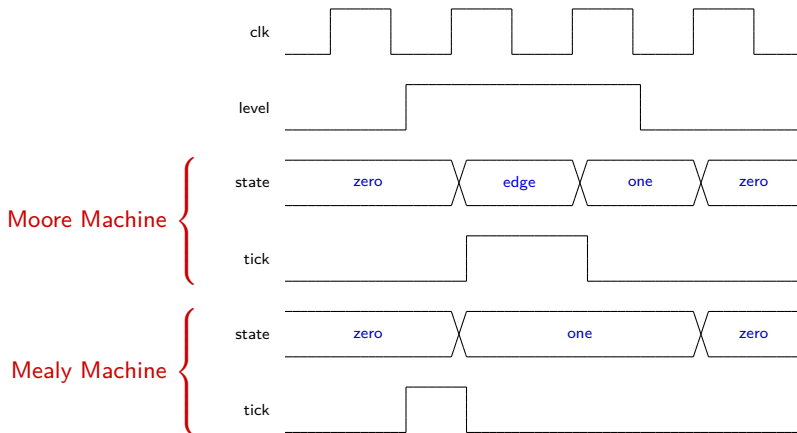

## State Diagram

 


## ASM Chart

 





## State Diagram

 

## ASM Chart

 


## Basic Block Diagram

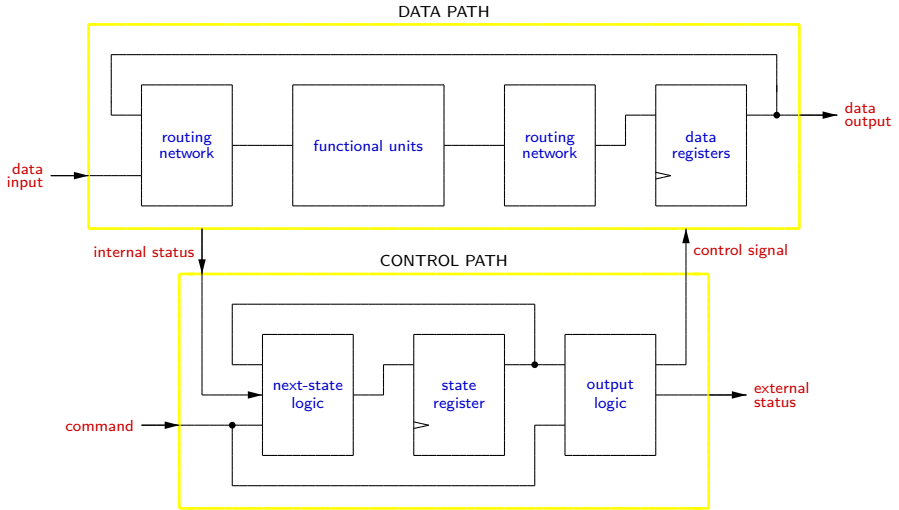



## Teil VI

# Top-Down Design of a Serial Adder



## Block Diagram

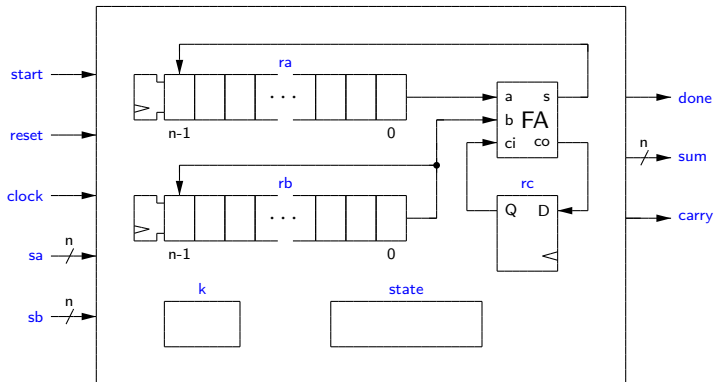



Example:  $10111010 + 01101100$

 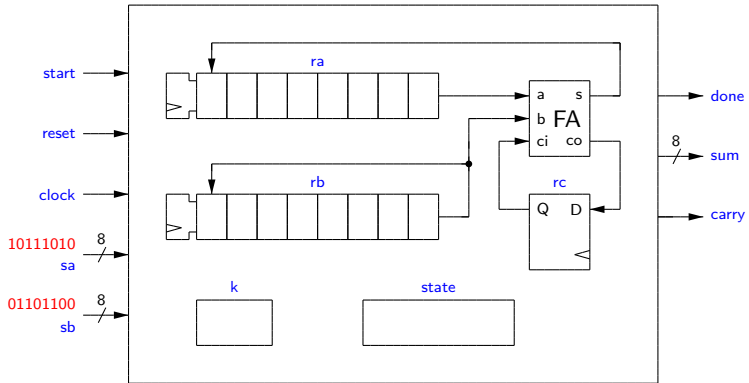



## Reset

 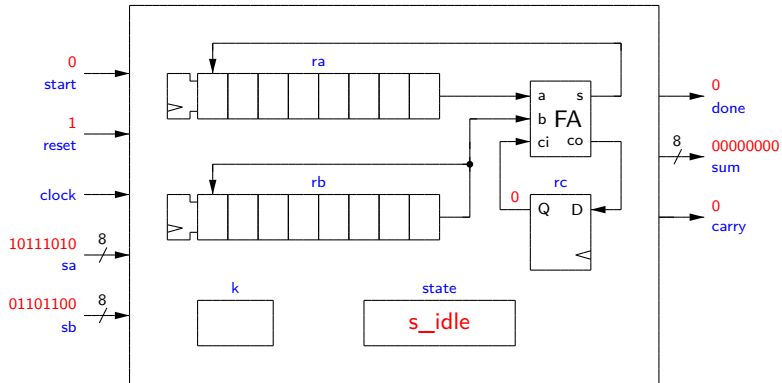

## Start

 
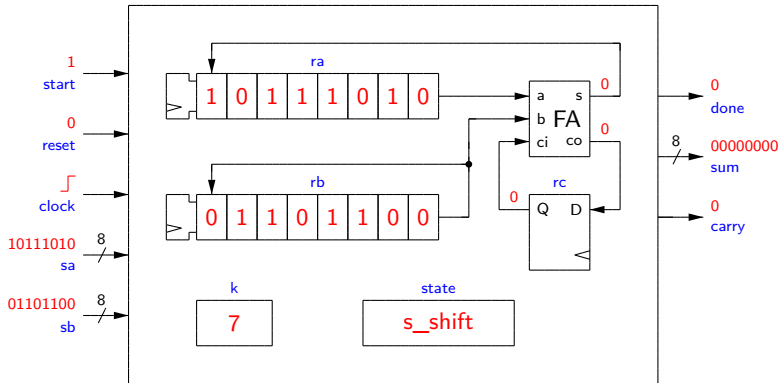


## Add and Shift

 
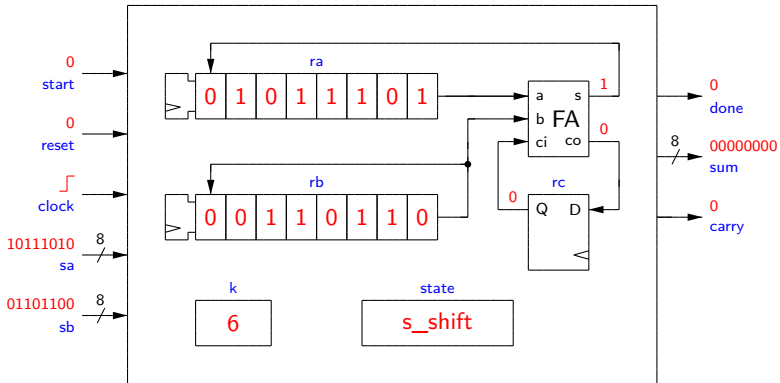






## Add and Shift

 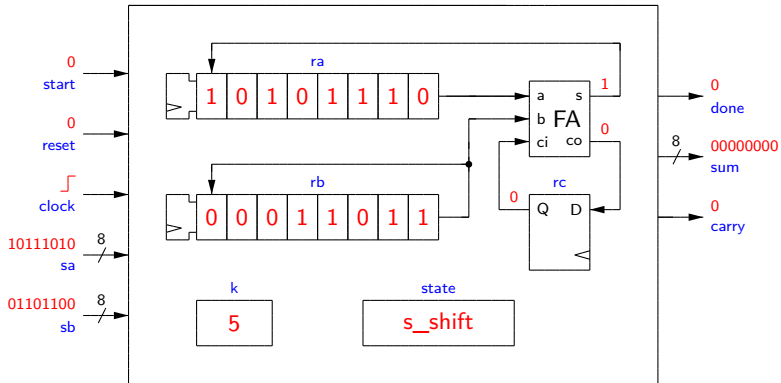



## Add and Shift

 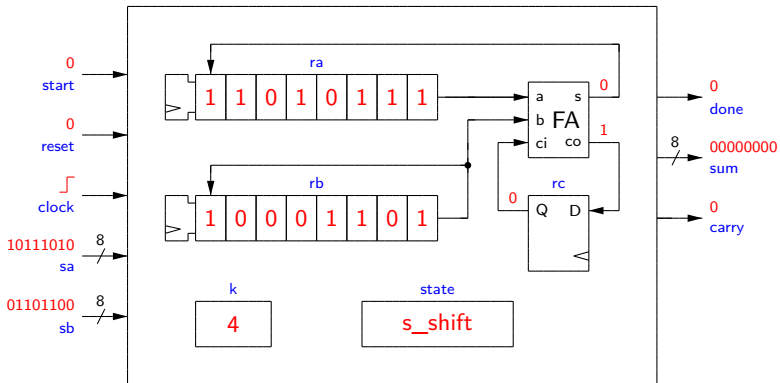



## Add and Shift

 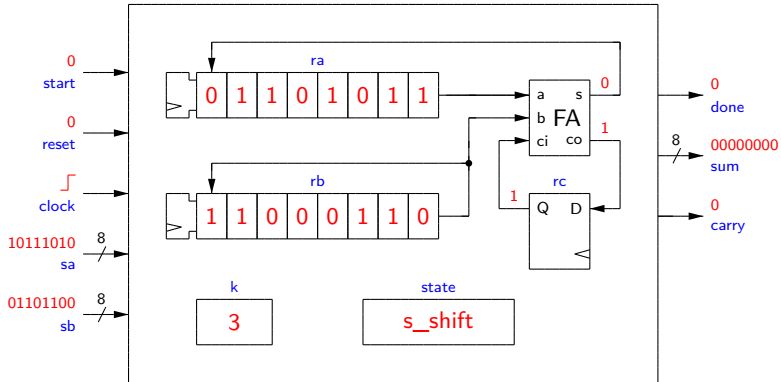



## Add and Shift

 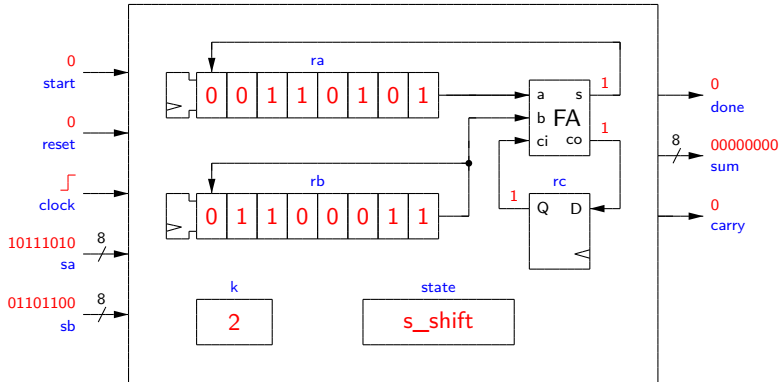



## Add and Shift

 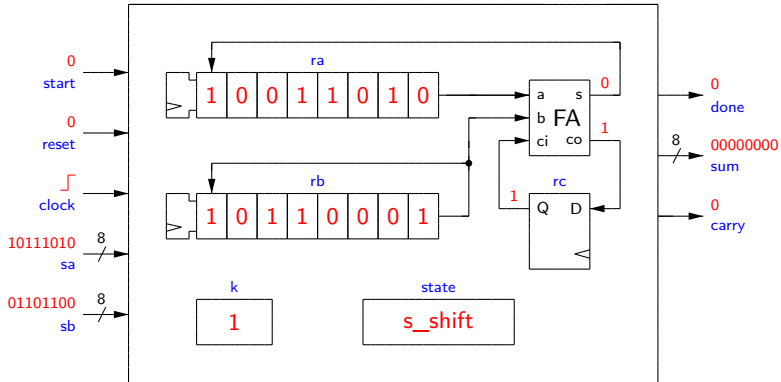


## Add and Shift

 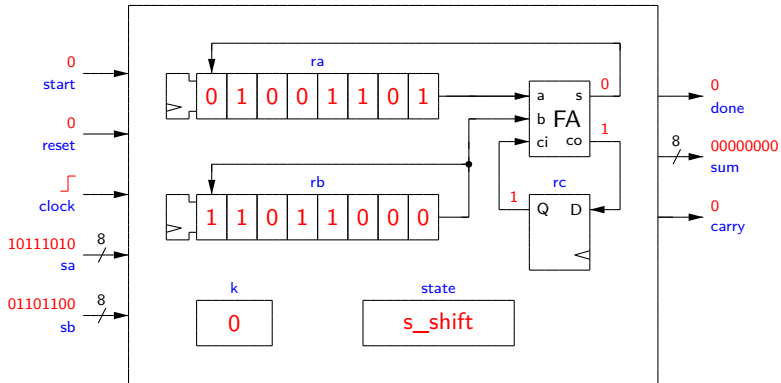

## Add and Shift

 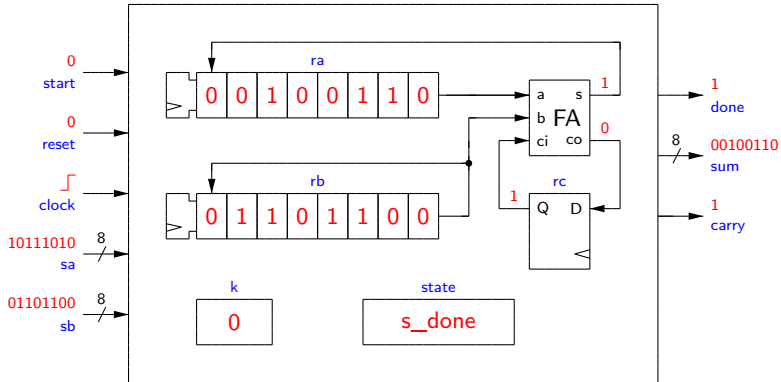

## ASM Chart

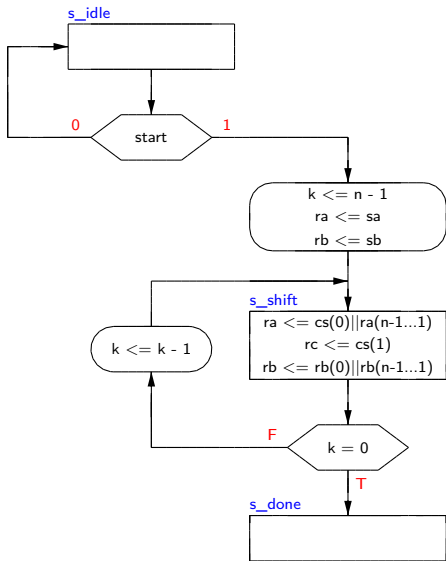

## VHDL-Code

```

control_unit: process(clk,reset)
begin
  if reset='1' then state <= s_idle;
                    rc <= '0';
  elsif clk'event and clk='1' then
    case state is
      when s_idle =>
        if start='1' then state <= s_shift;
                        k <= n - 1;
                        ra <= sa;
                        rb <= sb;
        end if;
      when s_shift =>
        ra <= cs(0)&ra(n-1 downto 1);
        rc <= cs(1);
        rb <= rb(0)&rb(n-1 downto 1);
        if k=0 then state <= s_done;
        else k <= k - 1;
        end if;
      when s_done =>
    end case;
  end if;
end process;
  
```